

Daily (formative) Quiz

- Compare current and voltage using a water hose as an analogy
- Does our classroom have a fuse box or a circuit breaker box? How do you know?
- Why did the microwave and Keurig lose power when they were both on?
- Why don't birds get electrocuted when they sit on power lines?



2.1 CONTROLLING THE FLOW OF ELECTRICAL CURRENT

RESISTANCE

measure of how **difficult** it is for electrons to flow through a substance

RESISTOR

device that provides resistance to the **flow of electrons**; often used to **control** electrical current

Resistance

- Resistance in electricity is like the size of the water pipe in the water analogy.



Unit & Abbreviation: Ohm (Ω)

Mathematical Notation: R

Resistors

- Electrons in a current always flow towards the positive end of the voltage source.
- Resistors decrease the amount of current flowing past them
- Examples:



Tungsten filament of a light bulb



"Neon" signs



Electric stove/ cooktop

Loads Act as Resistors

- The more resistance a material has, the more energy it gains from each passing electron
- This energy is often released as heat or light



Tungsten filament of a light bulb




"Neon" signs



Electric stove/ cooktop

Other Resistors

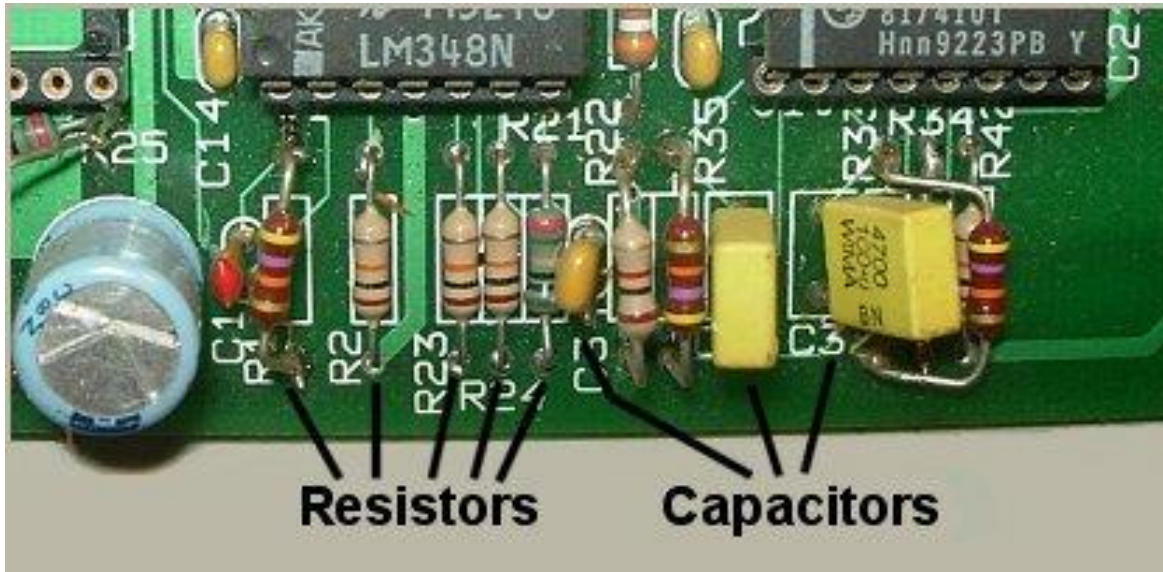


Their only purpose in life is to reduce current





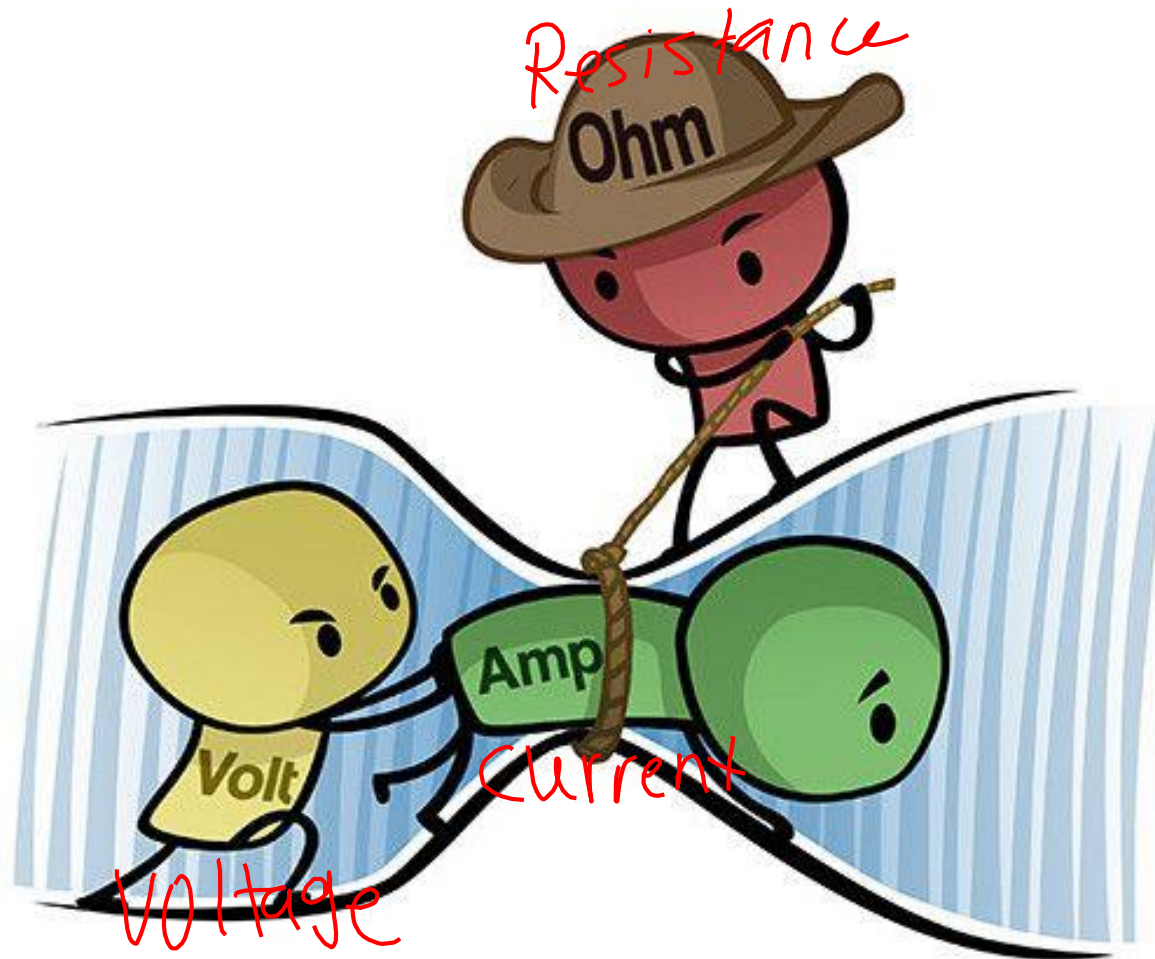
2.2 MODELLING AND MEASURING ELECTRICITY

How are Current, Voltage, and Resistance Related to Each Other?



Ohm's Law

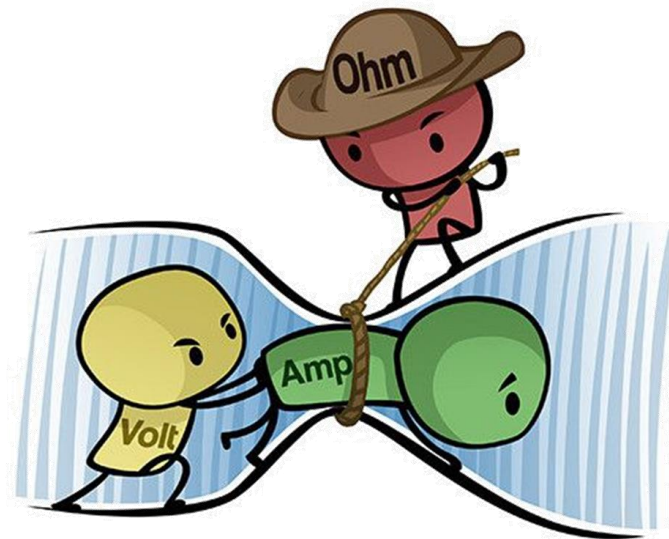- States that as long as temperature stays the same
 - if you increase the voltage in a circuit, the current also increases
 - if voltage stays the same but resistance increases, then current decreases



Ohm's Law

where, $V =$

$$V = I \times R$$

$I =$ Current (A)

$R =$ Resistance (Ω)

Voltage, Current, and Resistance

Quantity	Unit & abbreviation	Mathematical Notation
Voltage	Volts (v)	V
Current	Amps (A)	I
Resistance	Ohms (Ω)	R

Using Ohm's Law Formula

1. Identify known quantities
2. Identify unknown quantities
3. Use the appropriate formula
4. Solve the problem

Example 1

$$V = I \times R$$

What is the potential difference (voltage) across a 1500 Ω resistor carrying a current of 0.075 A?

$$R = 1500 \Omega$$

$$I = 0.075 \text{ A}$$

$$V = ?$$

$$V = 0.075 \text{ A}$$

$$\times 1500 \Omega$$

$$V = 112.5 \text{ V}$$

Answer = 112.5 V

Example 2

$$V = I \times R$$

An electric stove is connected to a 240 V outlet. The current through the stove is 20 A. Calculate the resistance in Ohms.

$$V = 240 \text{ V}$$

$$I = 20 \text{ A}$$

$$R = ?$$

$$\frac{V}{I} = \frac{I \times R}{I}$$

$$\frac{V}{I} = R$$

$$R = \frac{V}{I} = \frac{240 \text{ V}}{20 \text{ A}} = 12.0 \Omega$$

Answer = 12.0 Ω

Example 3

A 30 V battery creates a current through a 15 Ω resistor. What is the battery's current?

$$V = 30V$$

$$R = 15\ \Omega$$

$$I = ?$$

$$V = \frac{I R}{R}$$

$$I = \frac{V}{R} = \frac{30V}{15\ \Omega} = 2.0A$$

2.0 A

Example 4

A toaster with a resistance of $145\ \Omega$ is connected to a $120\ \text{V}$ wall outlet. What current will flow through the toaster?

0.83 A