

$$\underline{V = IR}$$

## Daily Quiz

1. What voltage is applied to a  $5.0 \Omega$  resistor if the current is  $1.5 \text{ A}$ ?
2. A voltage of  $80 \text{ V}$  is applied across a  $20 \Omega$  resistor. What is the current through the resistor?
3. The current running through a starter motor in a car is  $240 \text{ A}$ . If this motor is connected to a  $12 \text{ V}$  battery, what is the resistance of the motor?

$$V = IR$$

## Daily Quiz - Answers

1. What voltage is applied to a  $5.0 \Omega$  resistor if the current is  $1.5 \text{ A}$ ?

$$\begin{aligned} I &= 1.5 \text{ A} \\ R &= 5.0 \Omega \\ V &= ? \end{aligned}$$

$$V = I \times R$$

$$1.5 \times 5.0 =$$
$$\boxed{7.5 \text{ V}}$$

$$V = IR$$

## Daily Quiz - Answers

2. A voltage of 80 V is applied across a 20  $\Omega$  resistor. What is the current through the

resistor?  $V = I \times R$



$$I = \frac{V}{R} = \frac{80V}{20\Omega} = 4A$$

$$V = IR$$

## Daily Quiz - Answers

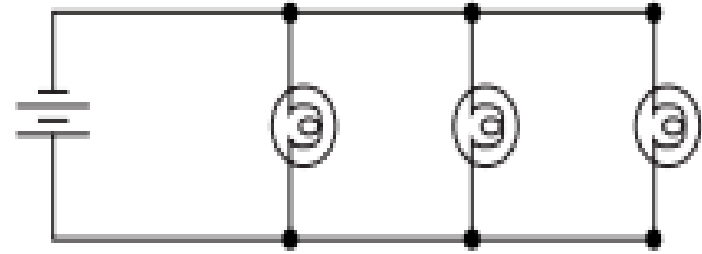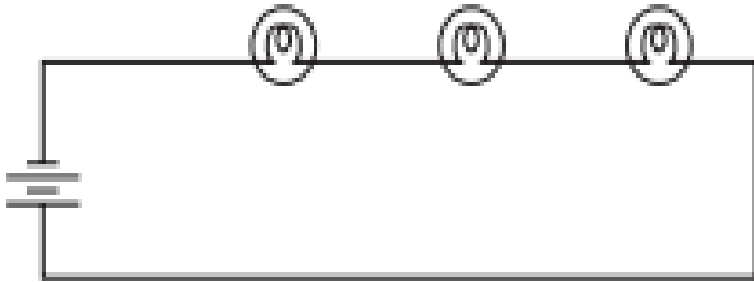3. The current running through a starter motor in a car is 240 A. If this motor is connected to a 12 V battery, what is the resistance of the motor?


$$\frac{12}{240} = \frac{240 \times R}{240}$$
$$0.05 = R$$
$$\underline{\Omega}$$



## 2.3 ANALYZING AND DRAWING ELECTRICAL CIRCUITS




# Virtual Circuit Challenge!!

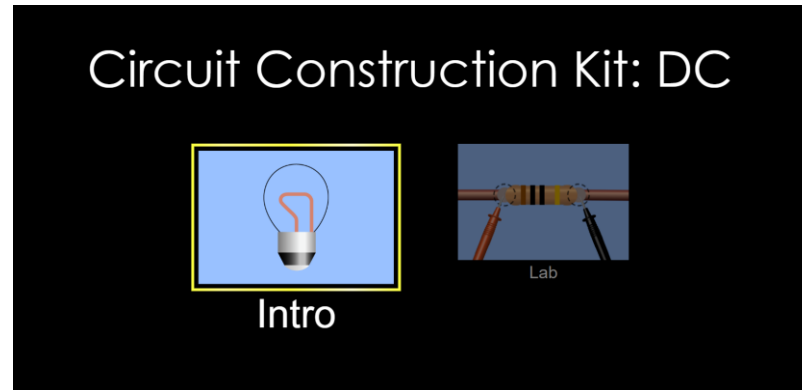


- Can you light a bulb?
- Can you increase or decrease the bulb's brightness?
- Can you make 2 bulbs in the same circuit have different brightness?
- Can you make a circuit where one bulb is switched off while another is on?
- Can you set your circuit on fire?
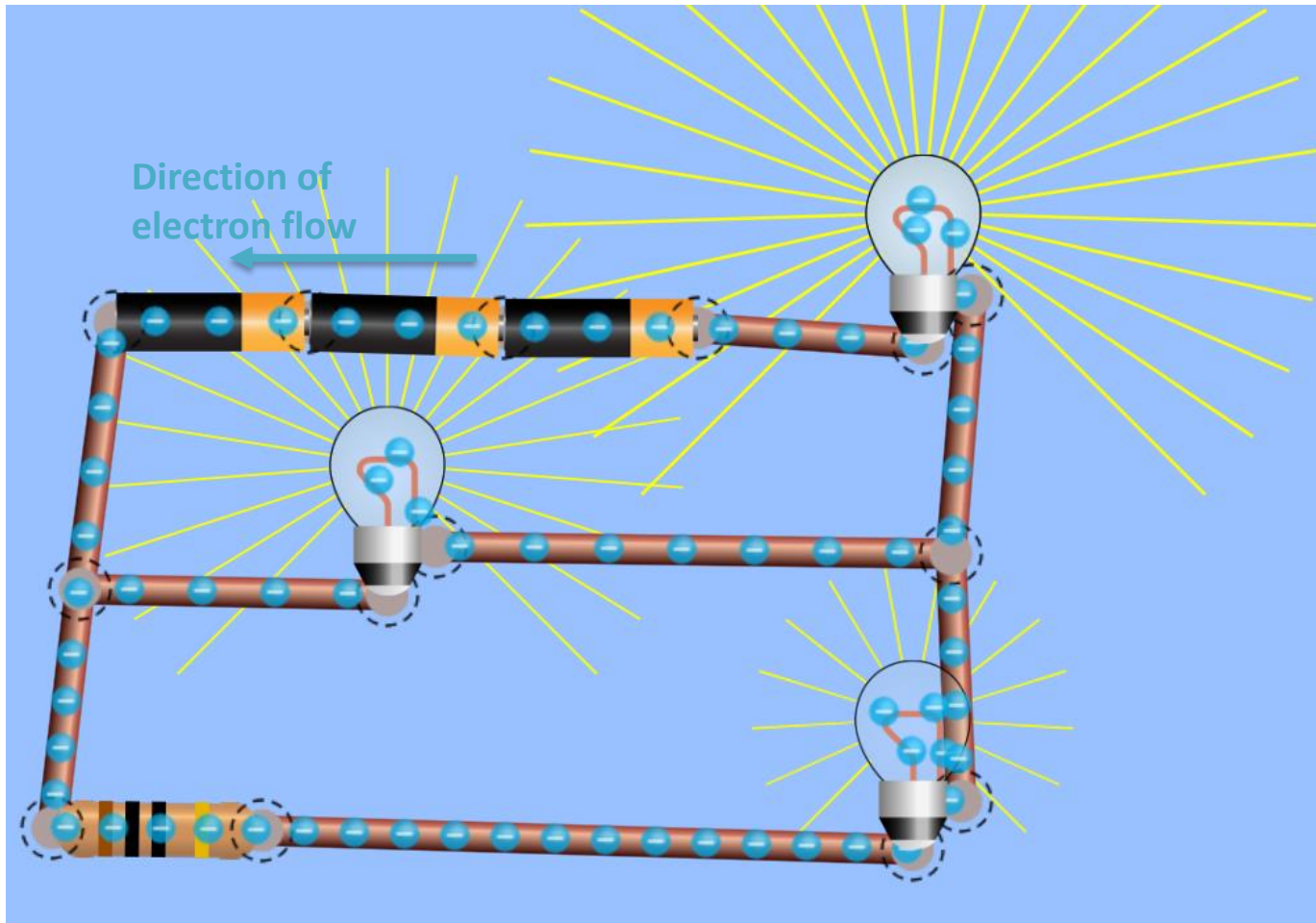
# Why is the brightness different for each bulb?





# Main Parts of a Circuit - Review

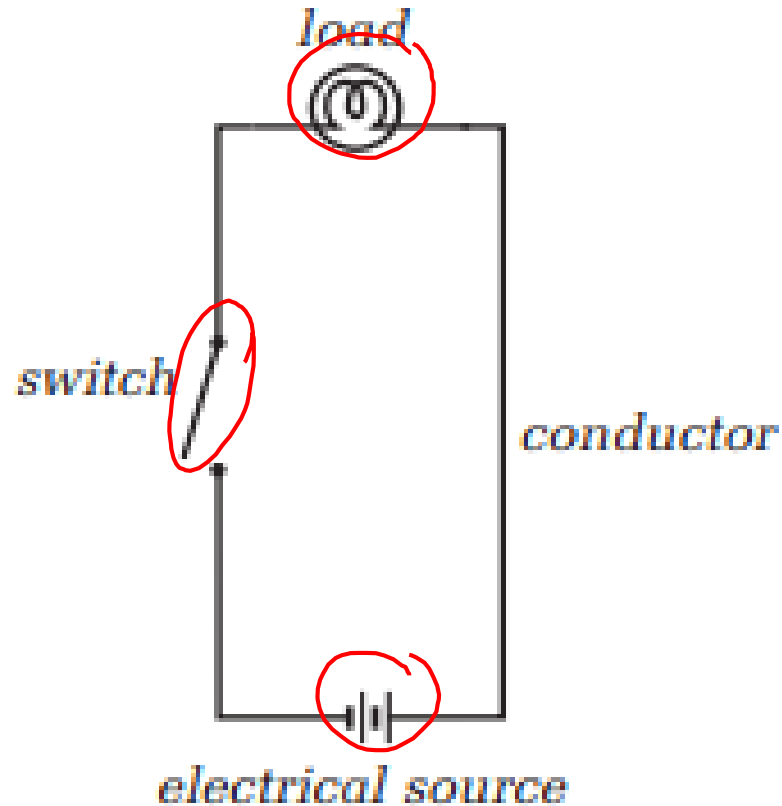

**Figure 2.22** The four basic parts of an electrical circuit

# Symbols for Circuit Diagrams



Symbol	Represents	Description
—	conductor ★	conducts electricity through circuit
— —	cell ★	stores electricity (large bar is positive)
—  —	battery ★	combination of cells
⊙	lamp ★	converts electricity to light
—⚡—	resistor ★	controls the amount of current in the circuit
—⚡—	switch ★	opens and closes circuit—allows current to flow
⊙A	ammeter ★	measures amount of current in circuit
⊙V	voltmeter ★	measures voltage across a device in a circuit
—⚡—	rheostat	variable resistor
⊙	motor	converts electricity to mechanical energy
—⚡—	fuse	melts if current in circuit is too high


You should memorize the starred ones!

# Rules for Drawing Circuit Diagrams

- use standard symbols (shown above) to show parts and connections
- electrons move from negative to positive
- All lines must be straight
- All corners must be 90° angles

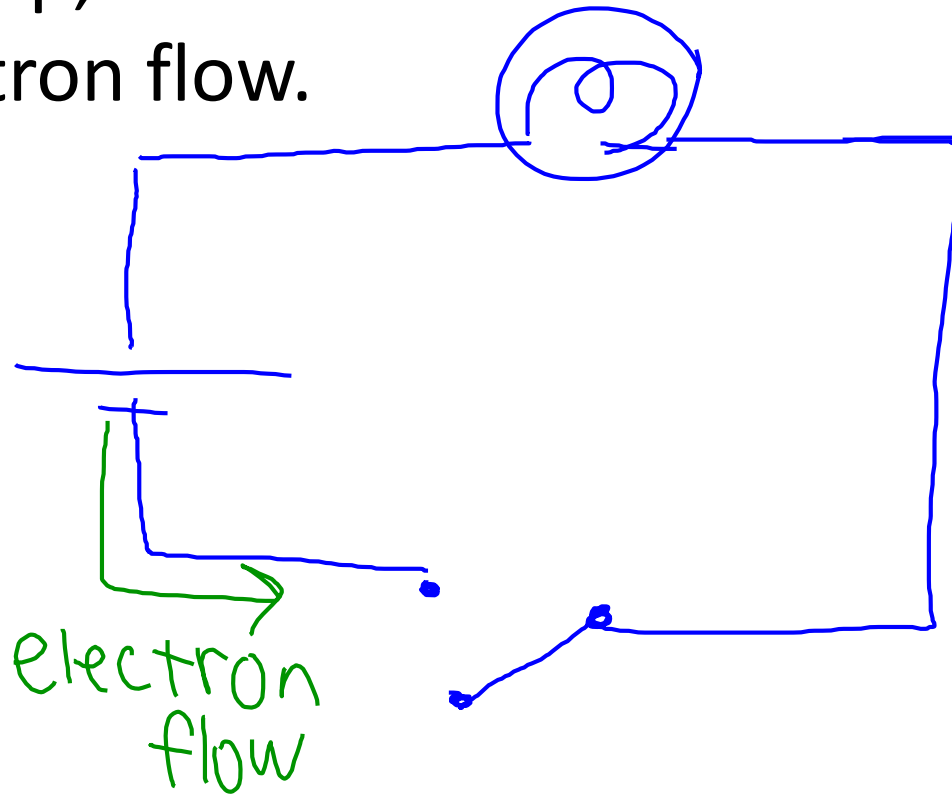
# Example 1

Draw a closed circuit diagram with one ~~battery~~<sup>cell</sup>, one lamp, and one switch. Indicate the direction of electron flow.




# Two Kinds of Circuits

## 1. Series Circuit

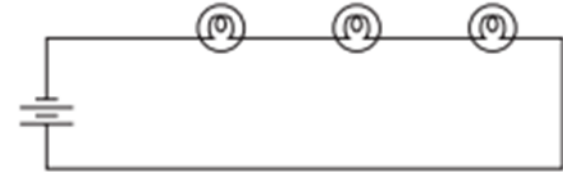


- only one pathway for the current
- all electrons travel through each component in the circuit
- adding loads increases resistance and decreases current.
- Current stops flowing if the circuit is broken at any point

# Series Circuits

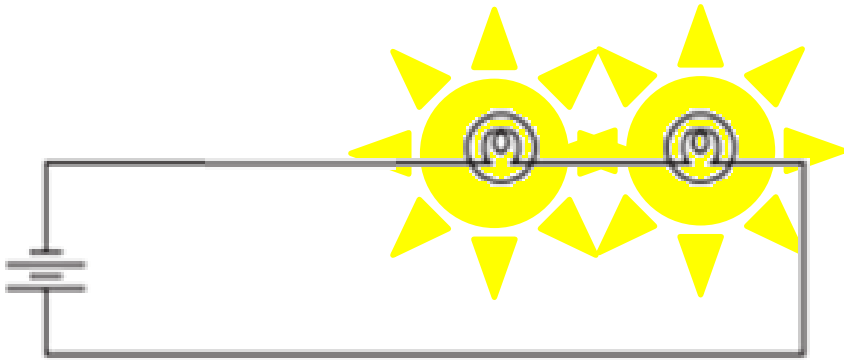

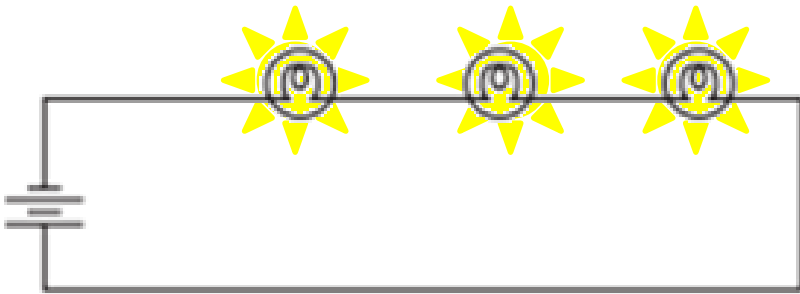
**If one bulb burns out, the other bulb will burn out**



**Adding bulbs will decrease the brightness of each bulb.**


# Two Kinds of Circuits

## 2. Parallel Circuit

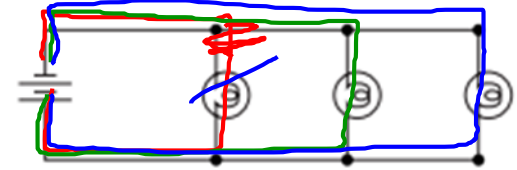


- more than one pathway for the current
- a break in one pathway does not affect other pathways in the circuit
- total current is split, with some electrons travelling through each branch, or part of the circuit.
- Adding resistance in one pathway does not affect resistance in other pathways.
- Most electrical devices in a house are connected in parallel

## 2. Parallel Circuits

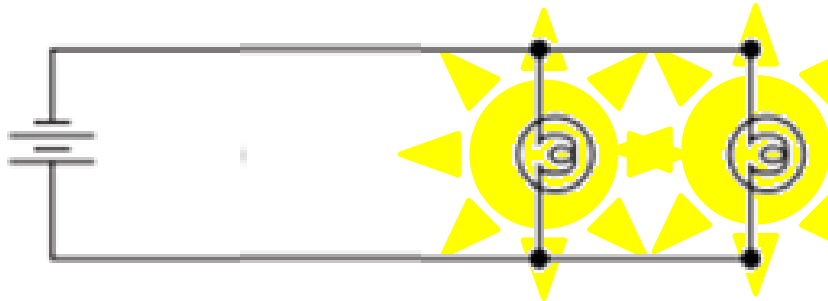

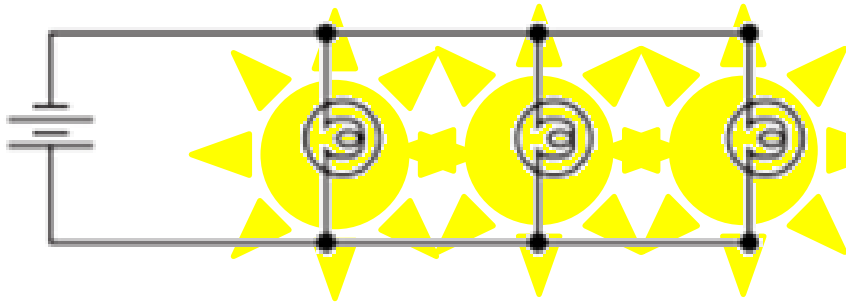
**If one bulb burns out, the other bulb is unaffected**



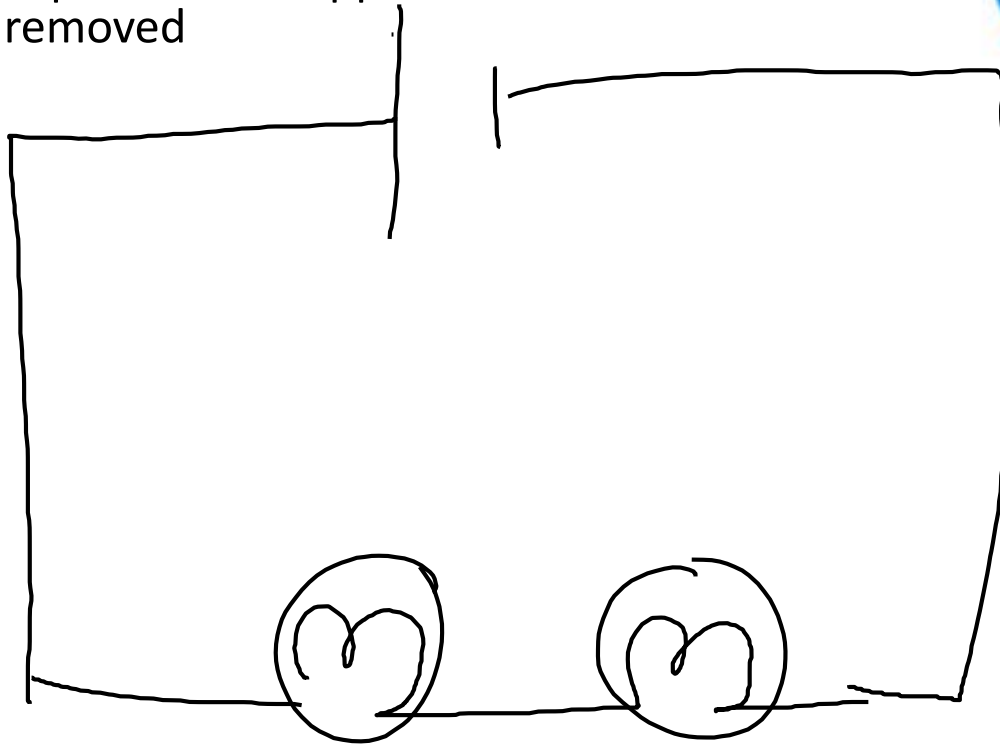**Adding bulbs will not affect the brightness of each bulb.**





- Draw
- Indicate direction of electron flow
- Label series or parallel
- Explain what happens if one bulb is removed




Series  
If one bulb is removed, the other goes out as well

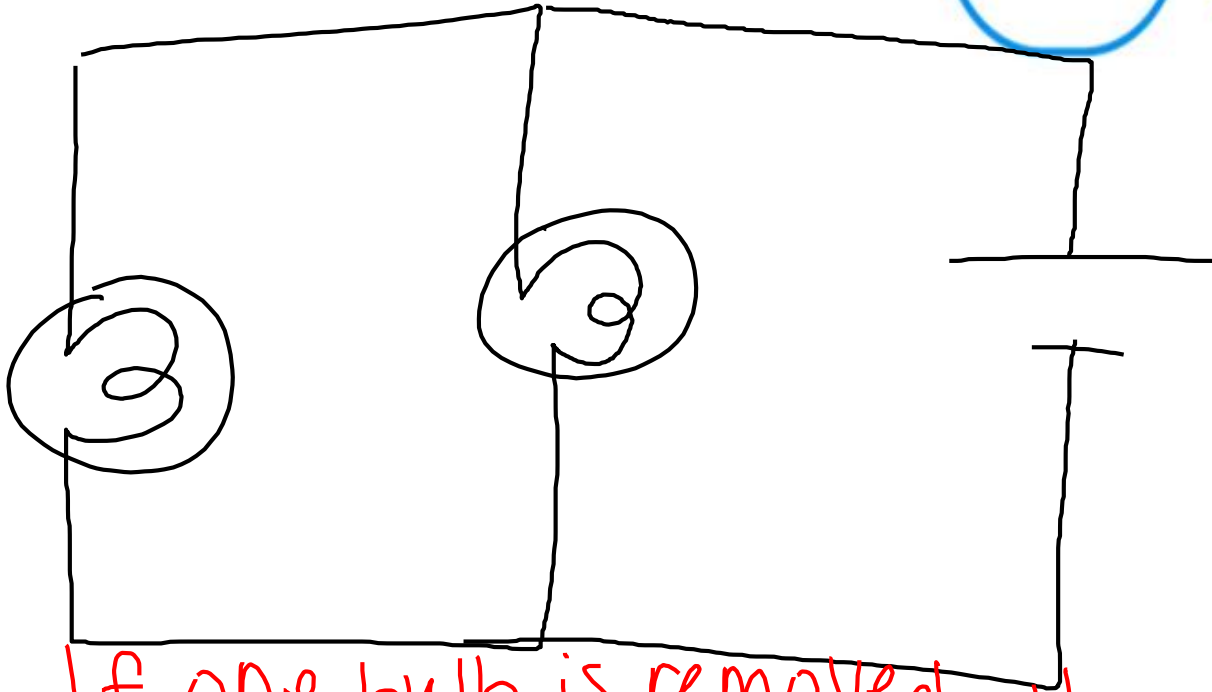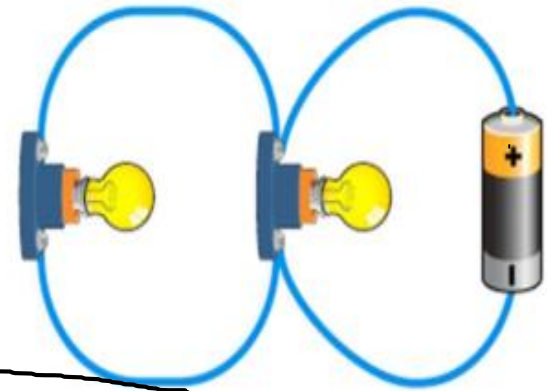- Draw
- Indicate direction of electron flow
- Label series or parallel
- Explain what happens if one bulb is removed




If one bulb is removed, the other stays on.

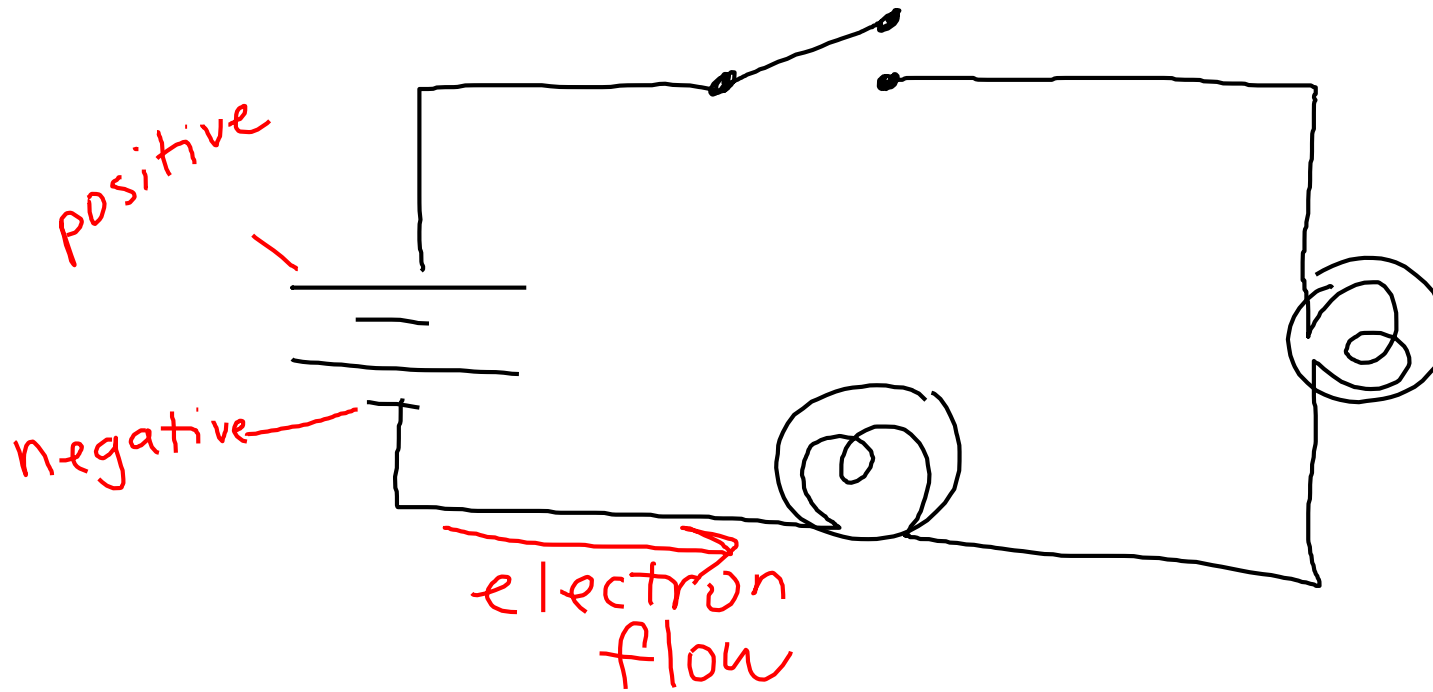c.) Draw a complete circuit that includes 2 cells and 2 lamps. The lamps are connected in series. A switch controls the entire circuit. Indicate the direction of electron flow.



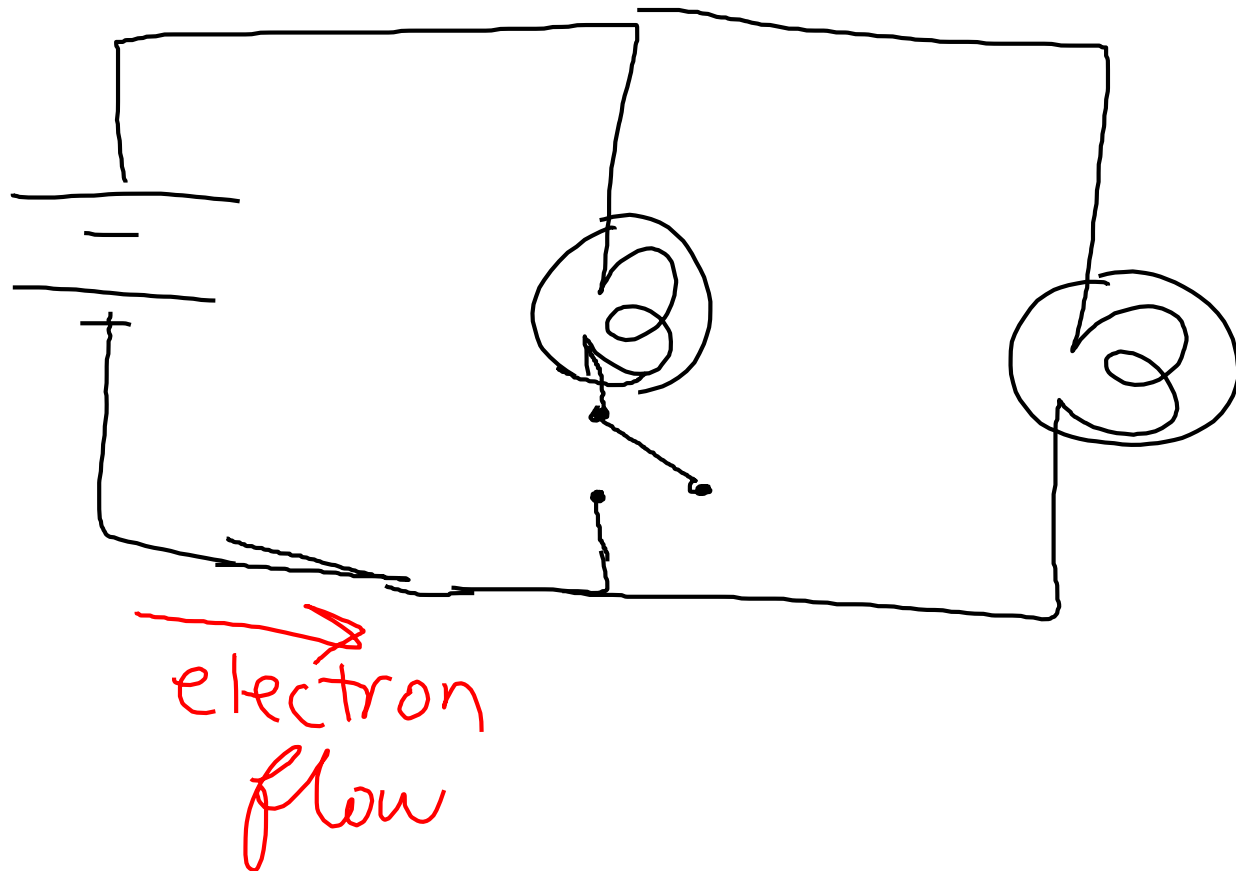
d.) Draw a complete circuit that includes 2 cells and 2 lamps. The lamps are connected in parallel. A switch controls the one of the lamps but does not affect the other. Indicate the direction of electron flow.



e.) A circuit was made with 3 cells, with a total voltage of 6.0 V. There were 2 lamps connected in parallel. An ammeter was connected right after the battery and read 5.8 A.

*negative end*

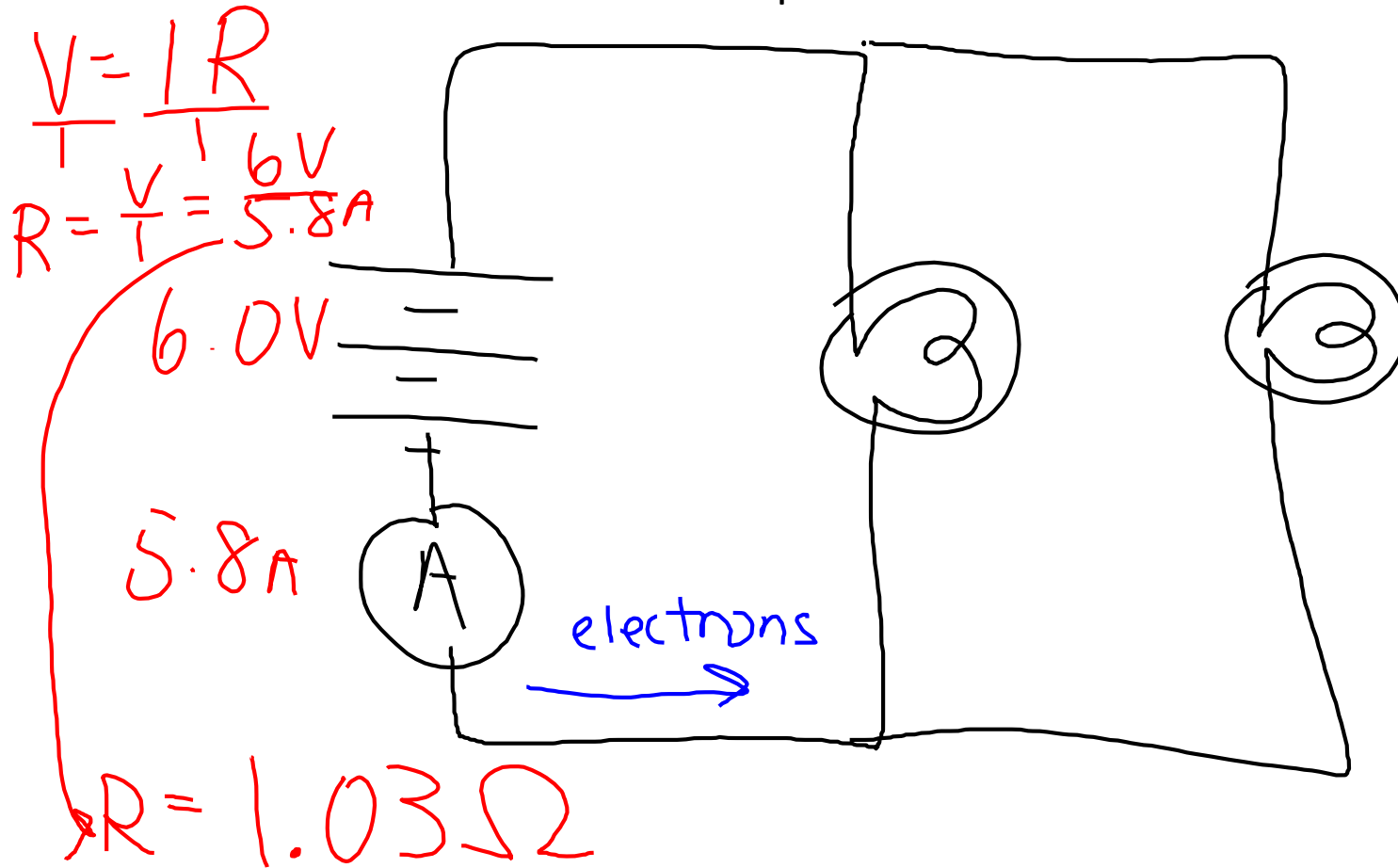
- Draw the circuit, indicate the direction of electron flow, and calculate the resistance of the circuit at the point of the ammeter.




each

f.) A circuit was made with 3 cells, with 2.0 V. There were 2 lamps and a motor connected in parallel. A resistor was connected right after the battery, and an ammeter was connected right after the resistor. The ammeter read 8.2 A.

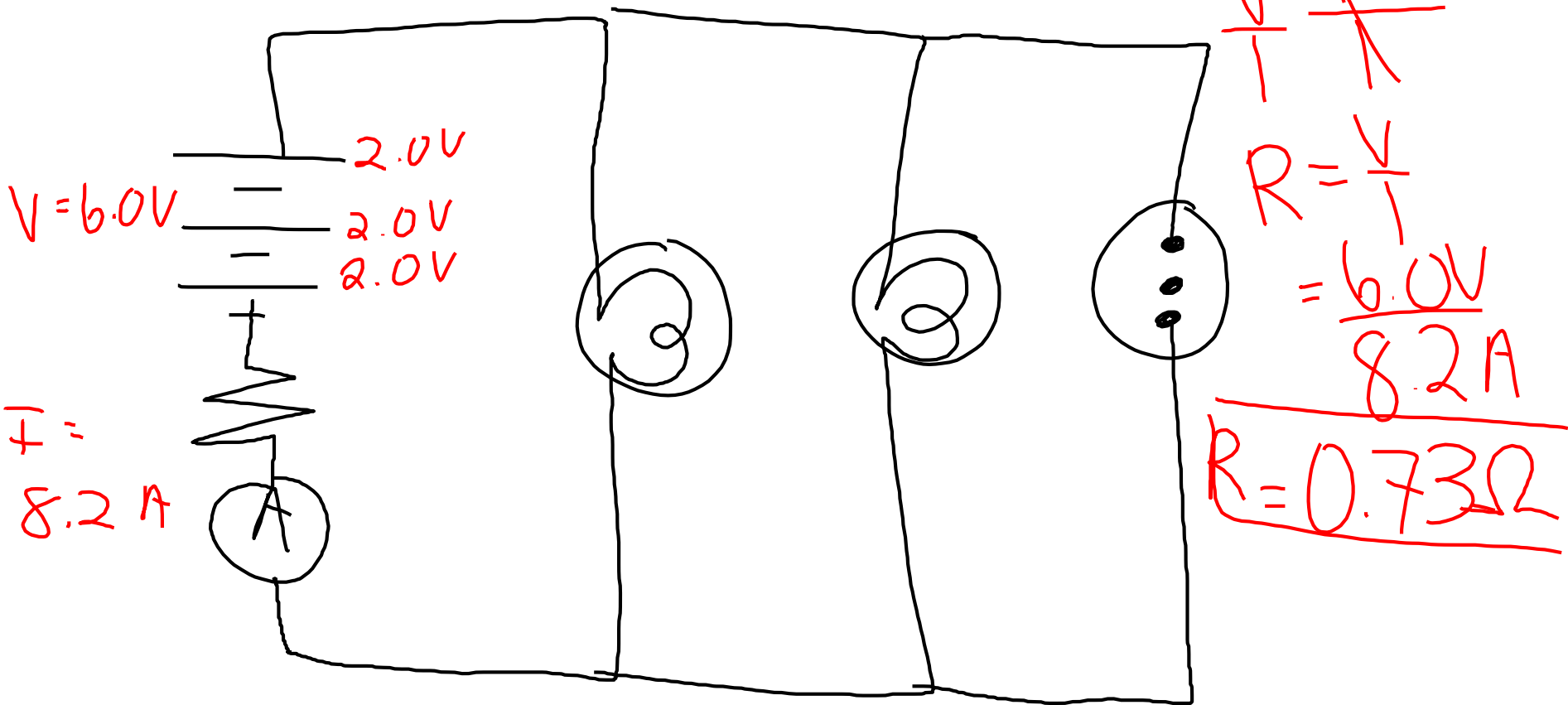- Draw the circuit, indicate the direction of electron flow, and calculate the resistance of the circuit at the point of the ammeter.




# Brightness of Lamps

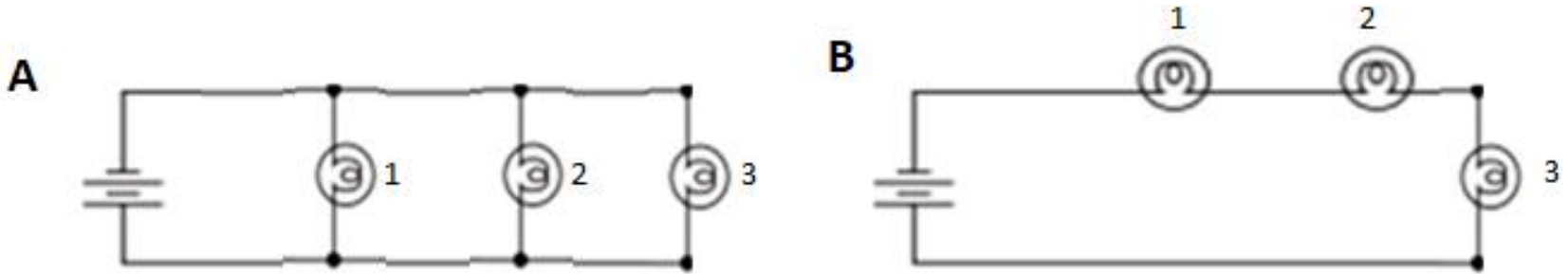

**1.** Each circuit shown above contains 3 lamps. In which circuit will the lamps be brighter?

"A" because it is a parallel circuit, so the flow of electrons is split

# Brightness of Lamps

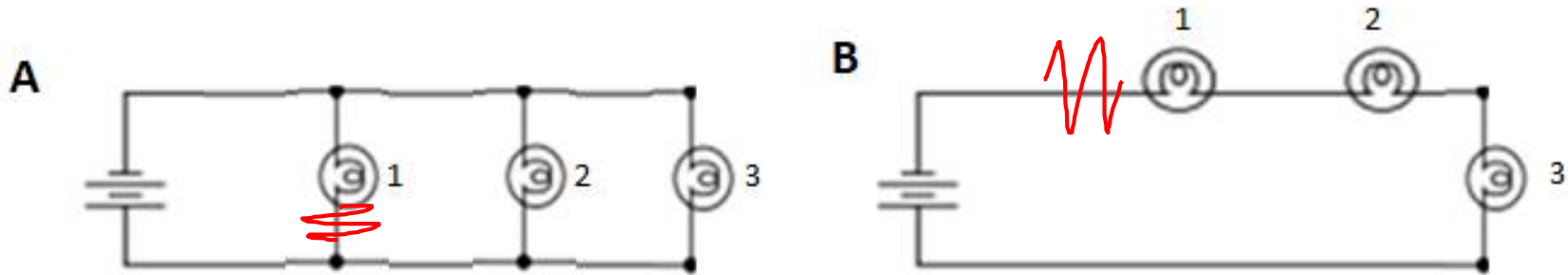

2. Draw a resistor just before Bulb 1 on each circuit. How is the brightness of the bulbs affected in:


-circuit A? Bulb A is dimmer than bulbs 2 + 3

-circuit B? All bulbs are dimmer than they were without the resistor.



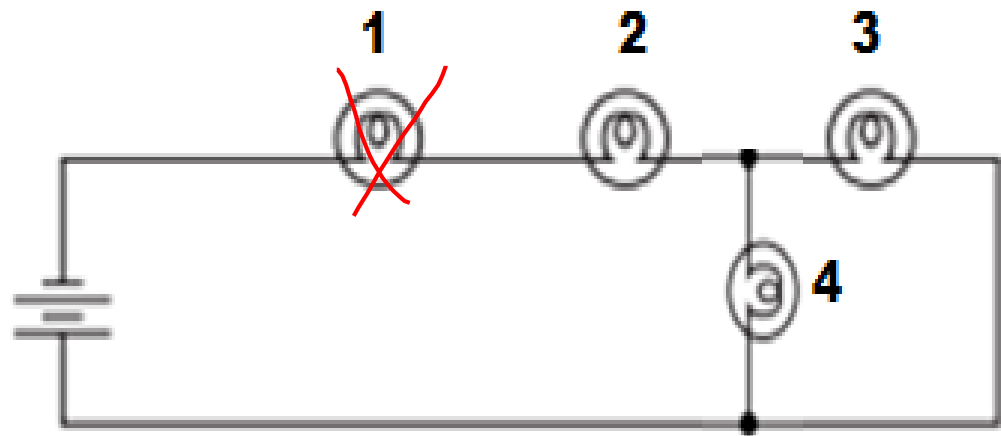
# Combination Circuits

- Some loads are connected in series and others in parallel




- If bulb 1 burns out: *All burn out*

# Combination Circuits

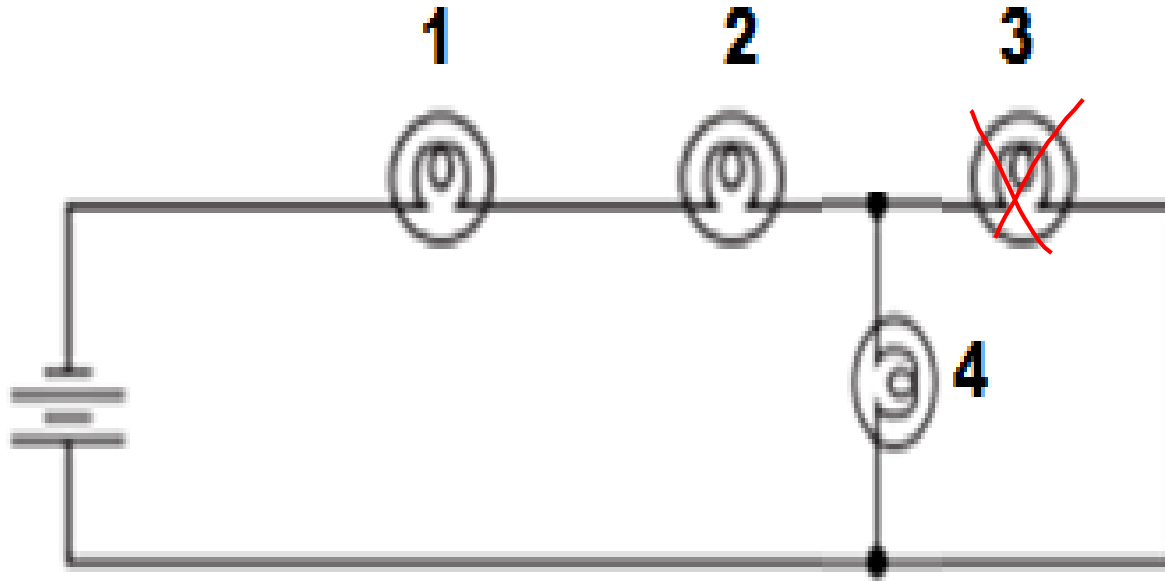


- If bulb 3 burns out: *Bulbs 1, 2, 4*  
*Stay lit*

# Combination Circuits

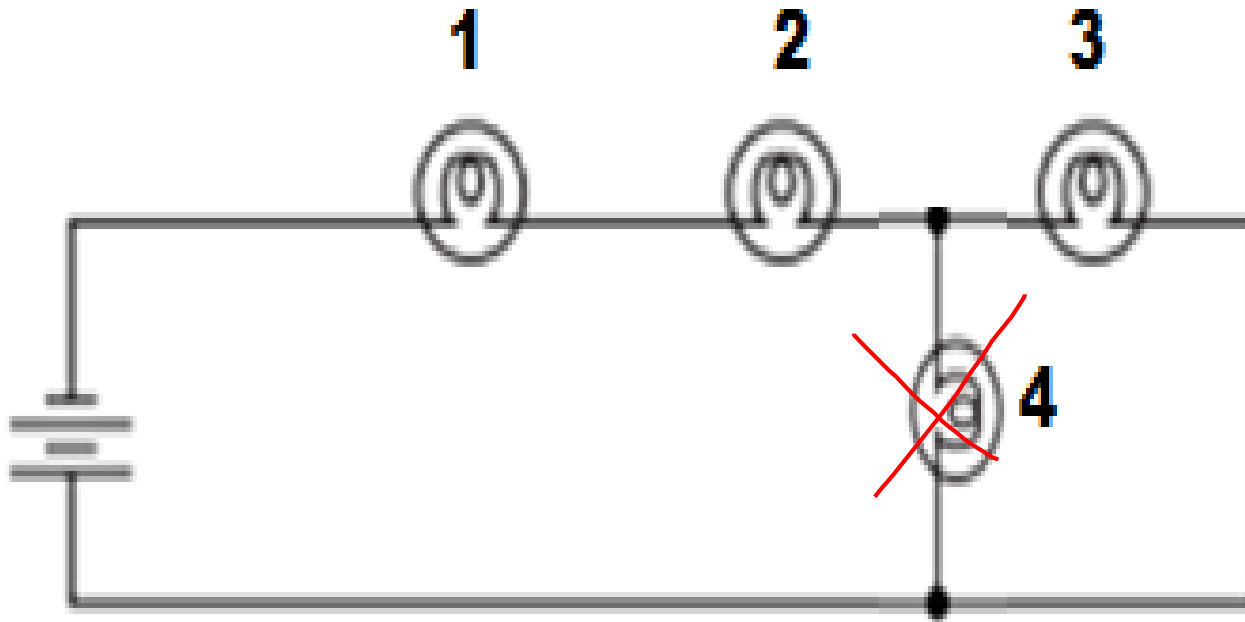

- If bulb 4 burns out: 1, 2, 3 stay lit


# Combination Circuits

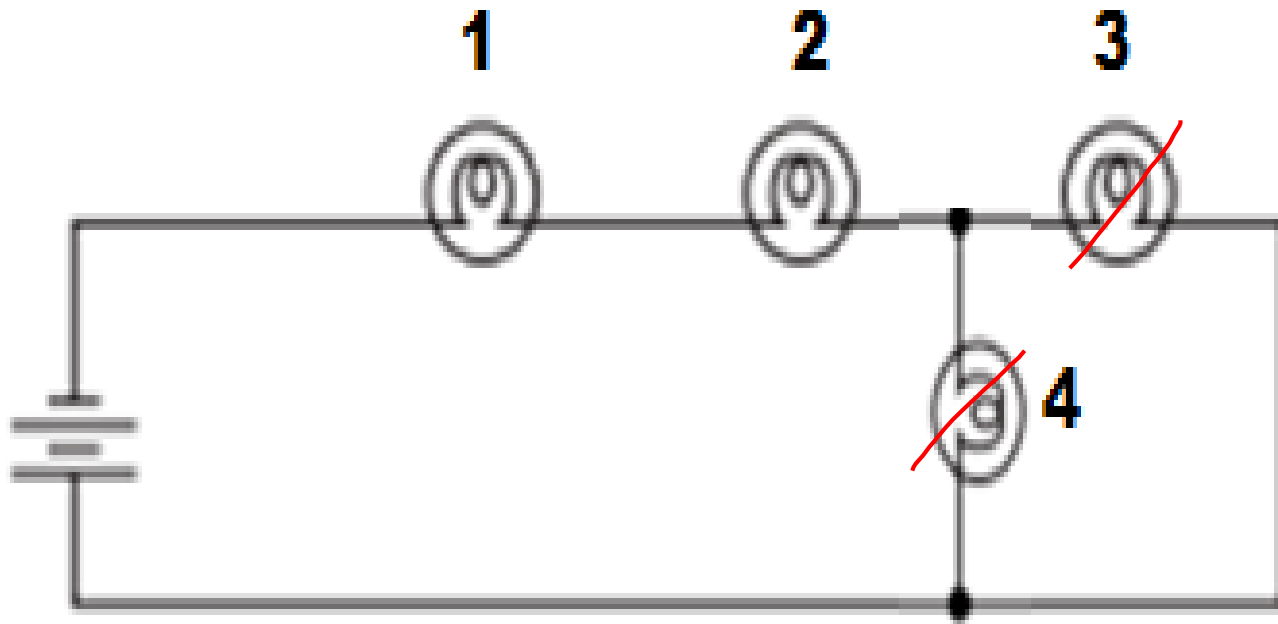

- If bulbs 3 & 4 burn out:  
*1 and 2 burn out also*
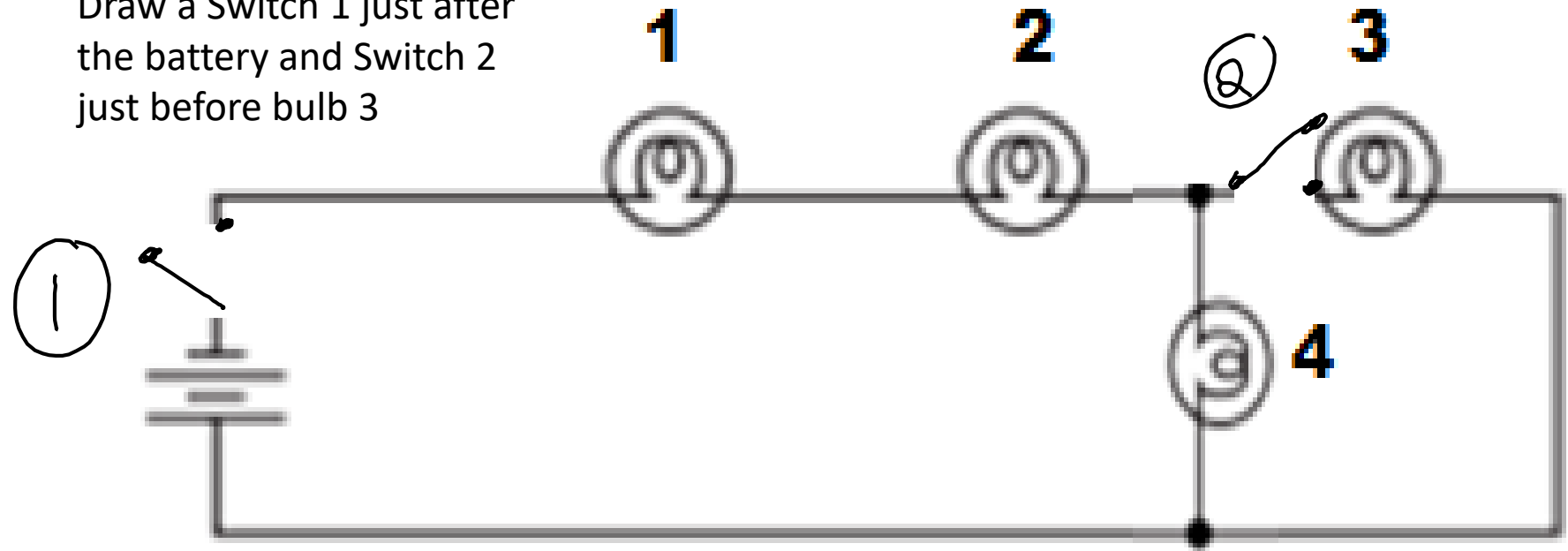
# Combination Circuits

Draw a Switch 1 just after the battery and Switch 2 just before bulb 3




How will the lamps be affected if switch 1 is open and Switch 2 is closed?

No complete circuit, so no bulbs lit
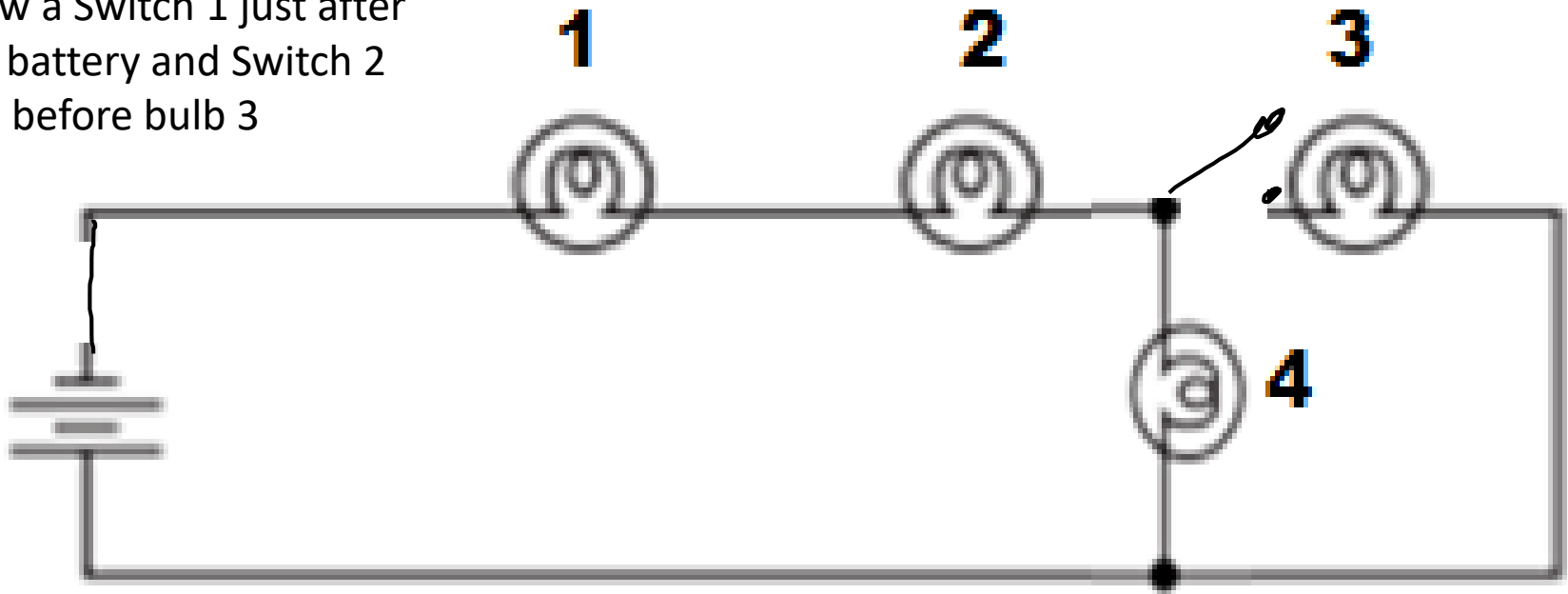
# Combination Circuits

Draw a Switch 1 just after the battery and Switch 2 just before bulb 3



How will the lamps be affected if switch 1 is closed and Switch 2 is open?

1, 2, & 4 will be lit but lamp 3 will not

# ✓ Check Your Understanding

Make sure you label  
your lamps


- Draw a circuit made with a 3-cell battery and 3 lamps. Lamp 1 is connected in parallel with lamp 3. Lamp 2 is connected in series with lamps 1 and 3. A switch controls the entire circuit.



- Draw a circuit that contains two motors and a lamp, connected in parallel. Include two switches: one to operate the lamp and one to control the whole circuit.


The circuit below has four bulbs (A-D) and four switches (1-4).

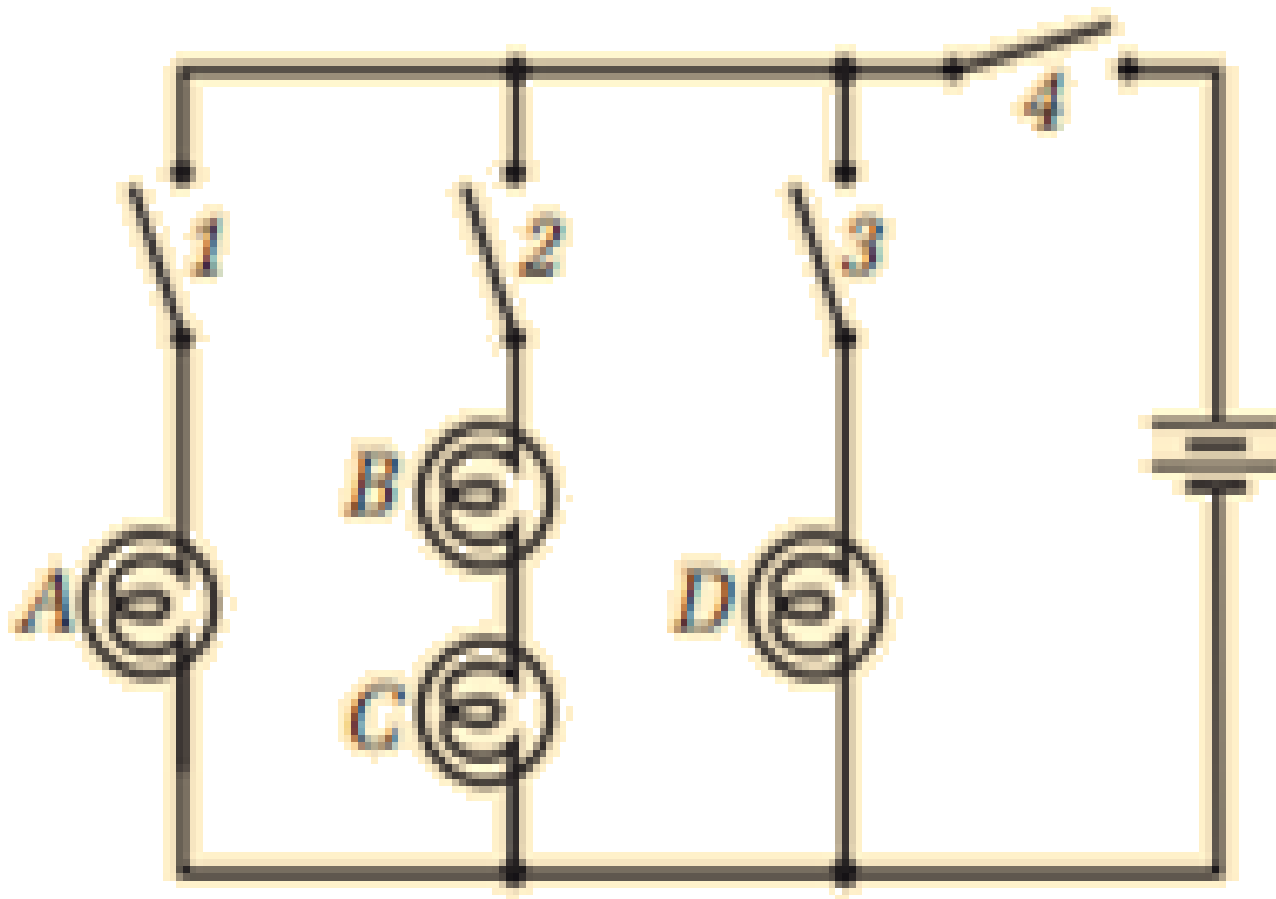a.) Which switch(es) should be closed to light bulbs A and D only? \_\_\_\_\_




The circuit below has four bulbs (A-D) and four switches (1-4).

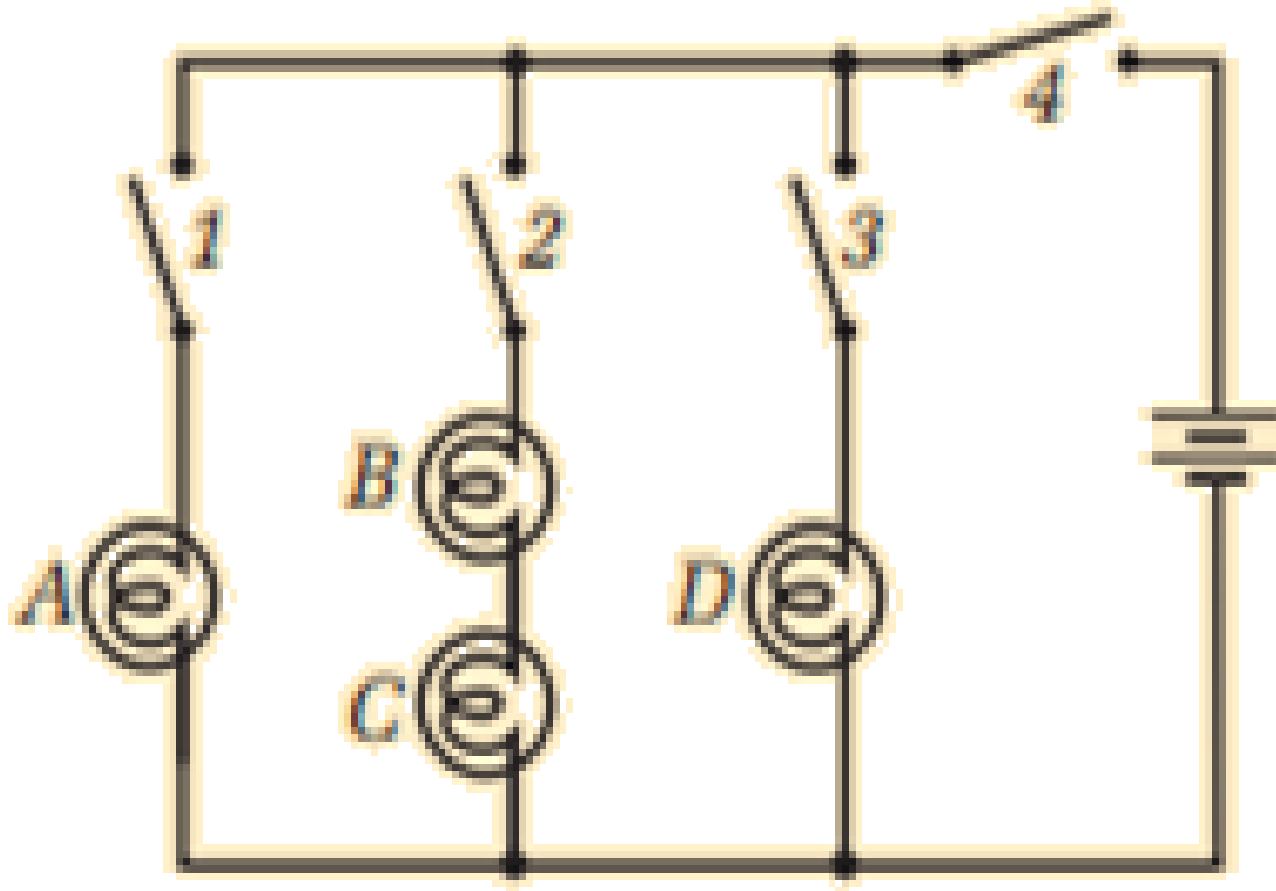b.) Which switch(es) should be closed to light bulb A only? \_\_\_\_\_




The circuit below has four bulbs (A-D) and four switches (1-4).

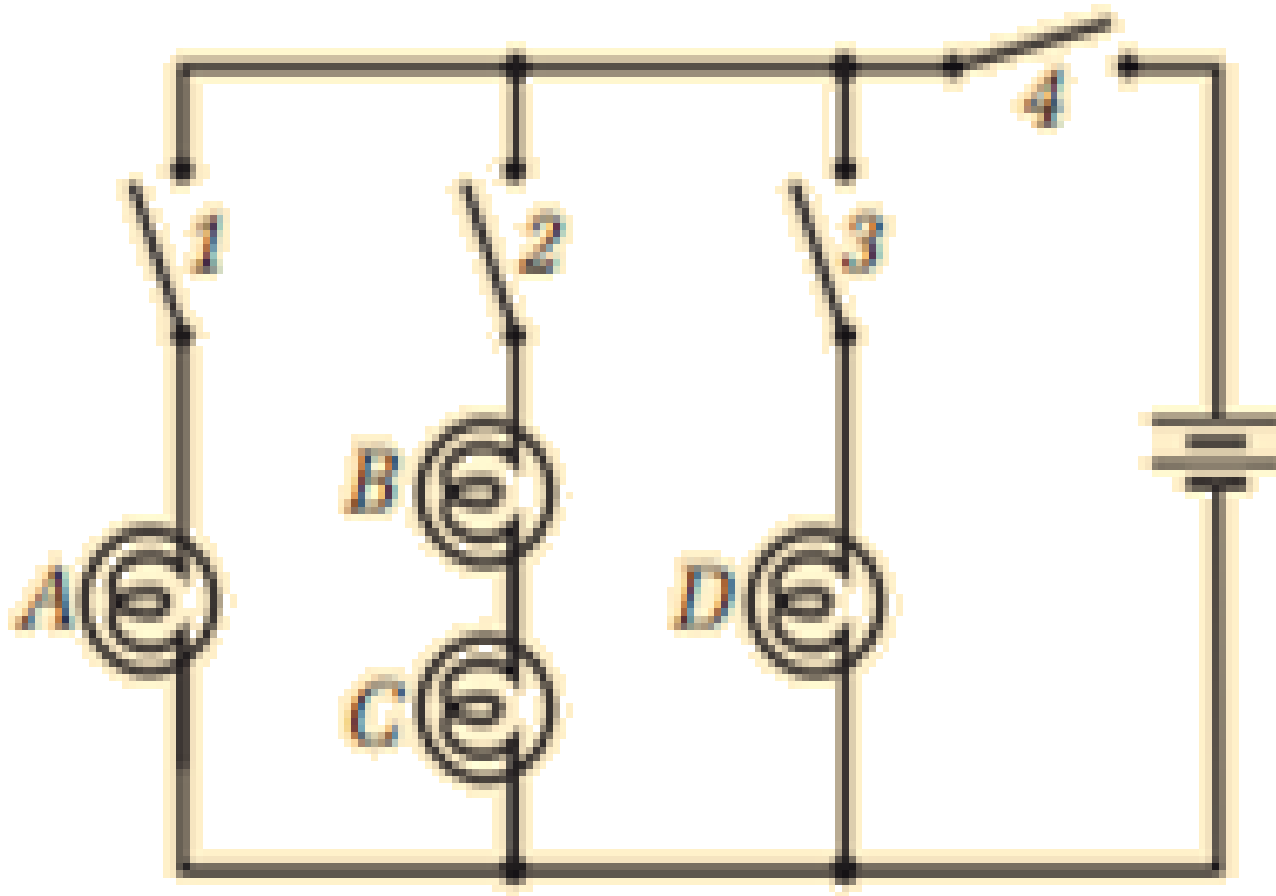c.) Which switch(es) should be closed to light bulbs B and C only? \_\_\_\_\_




The circuit below has four bulbs (A-D) and four switches (1-4).

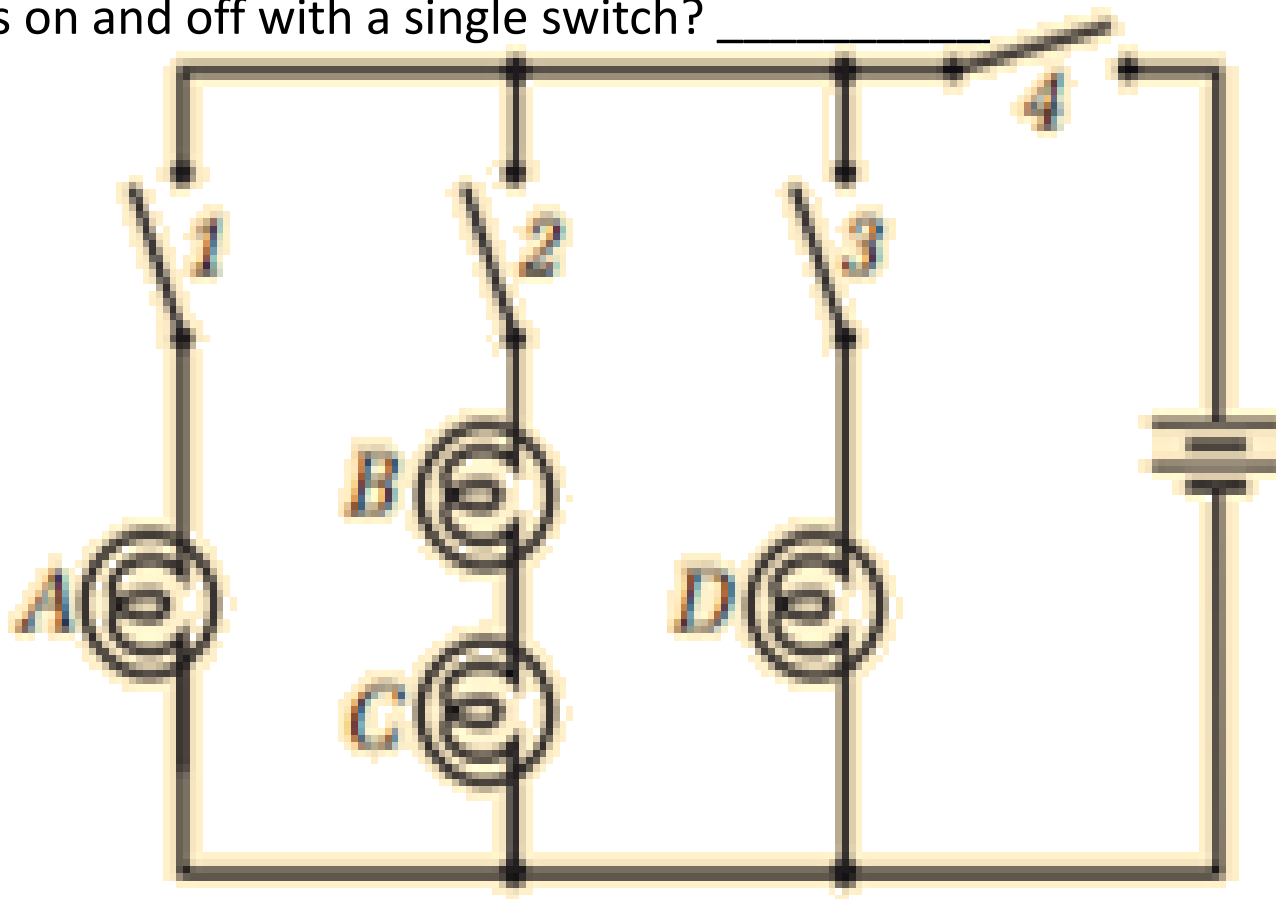d.) How would you organize the switches so that you could turn all the lights on and off with a single switch? \_\_\_\_\_



The circuit below has four bulbs (A-D) and four switches (1-4).

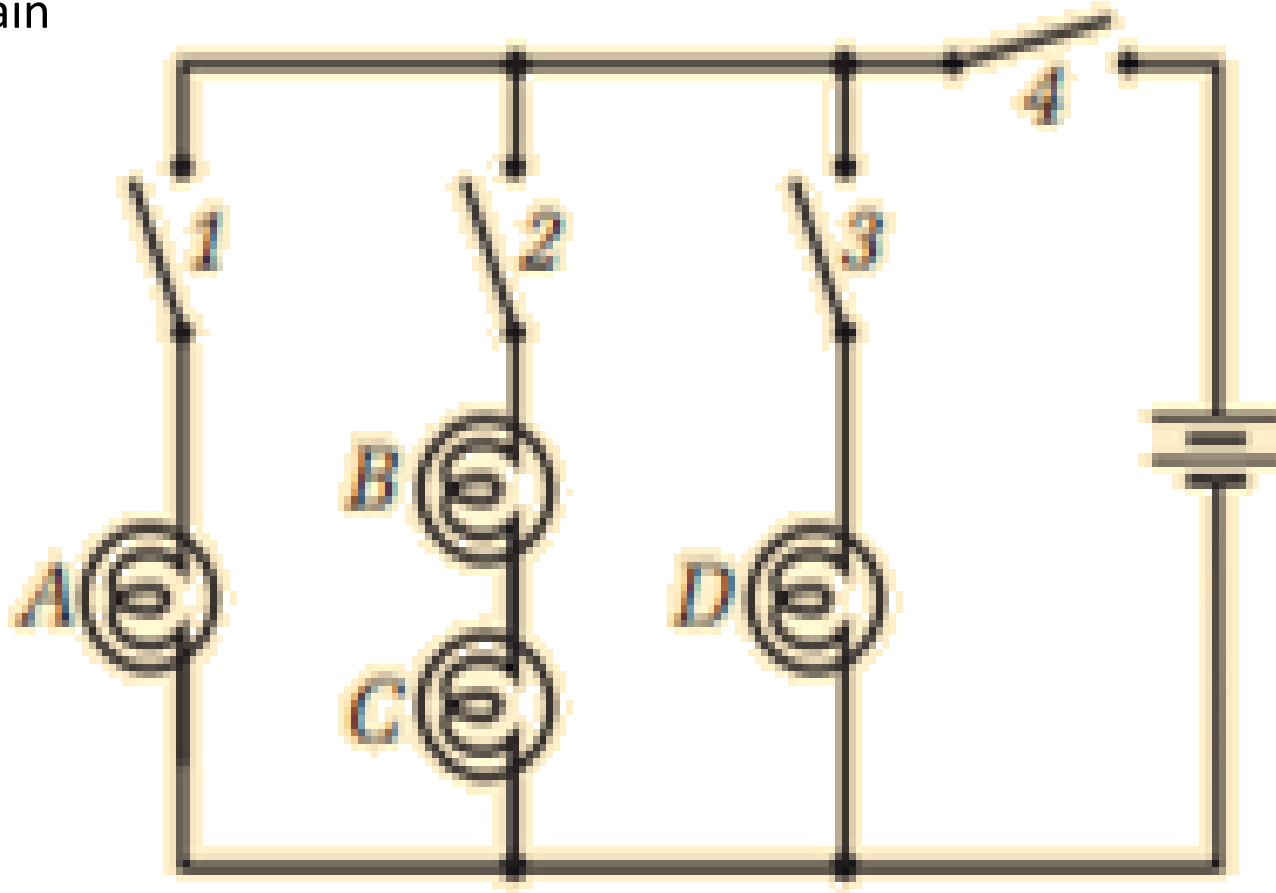e.) Is it possible to operate bulbs B and C independently of each other? Explain



4. A circuit was made with 3 cells, each with a voltage of 2.0 V. There were 2 lamps connected in parallel. An ammeter was connected right after the battery and read 5.8 A. There was also a resistor connected in series with both lamps.

- Draw the circuit and indicate the direction of electron flow
- Calculate the resistance of the circuit at the point of the ammeter