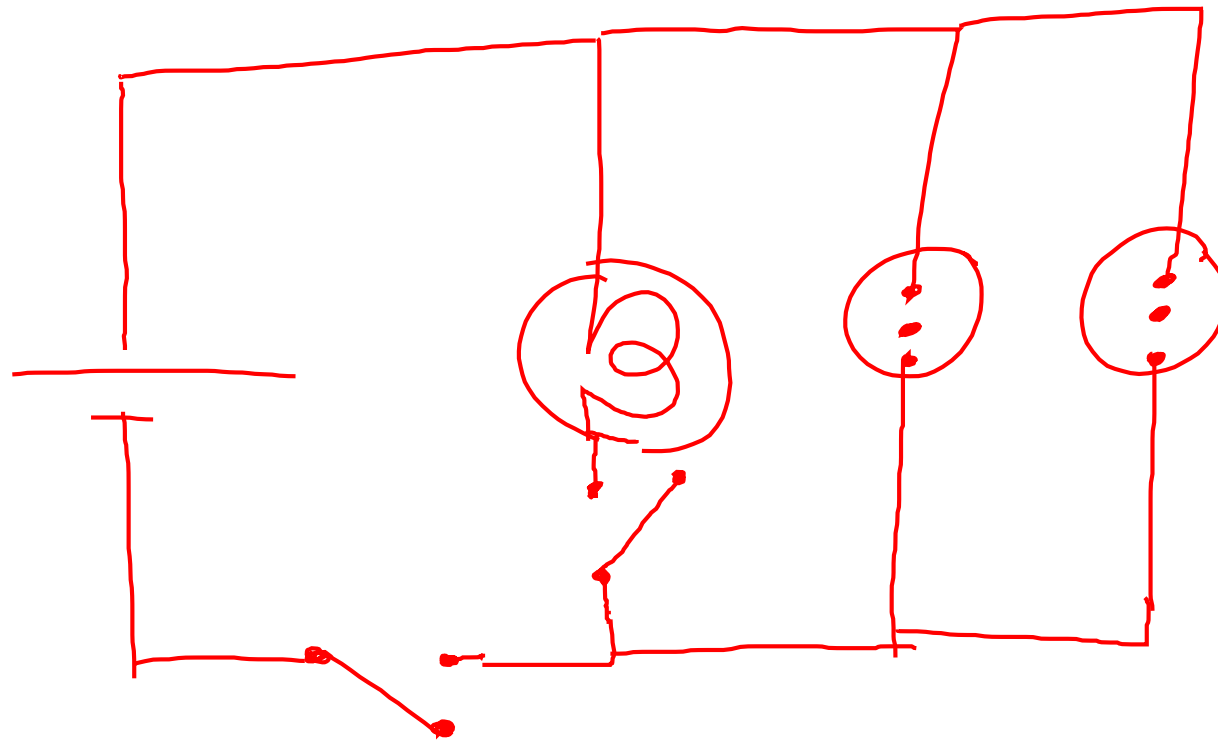



✓ Check Your Understanding

- Draw a circuit that contains two motors and a lamp, connected in parallel. Include two switches: one to operate the lamp and one to control the whole circuit.



The circuit below has four bulbs (A-D) and four switches (1-4).

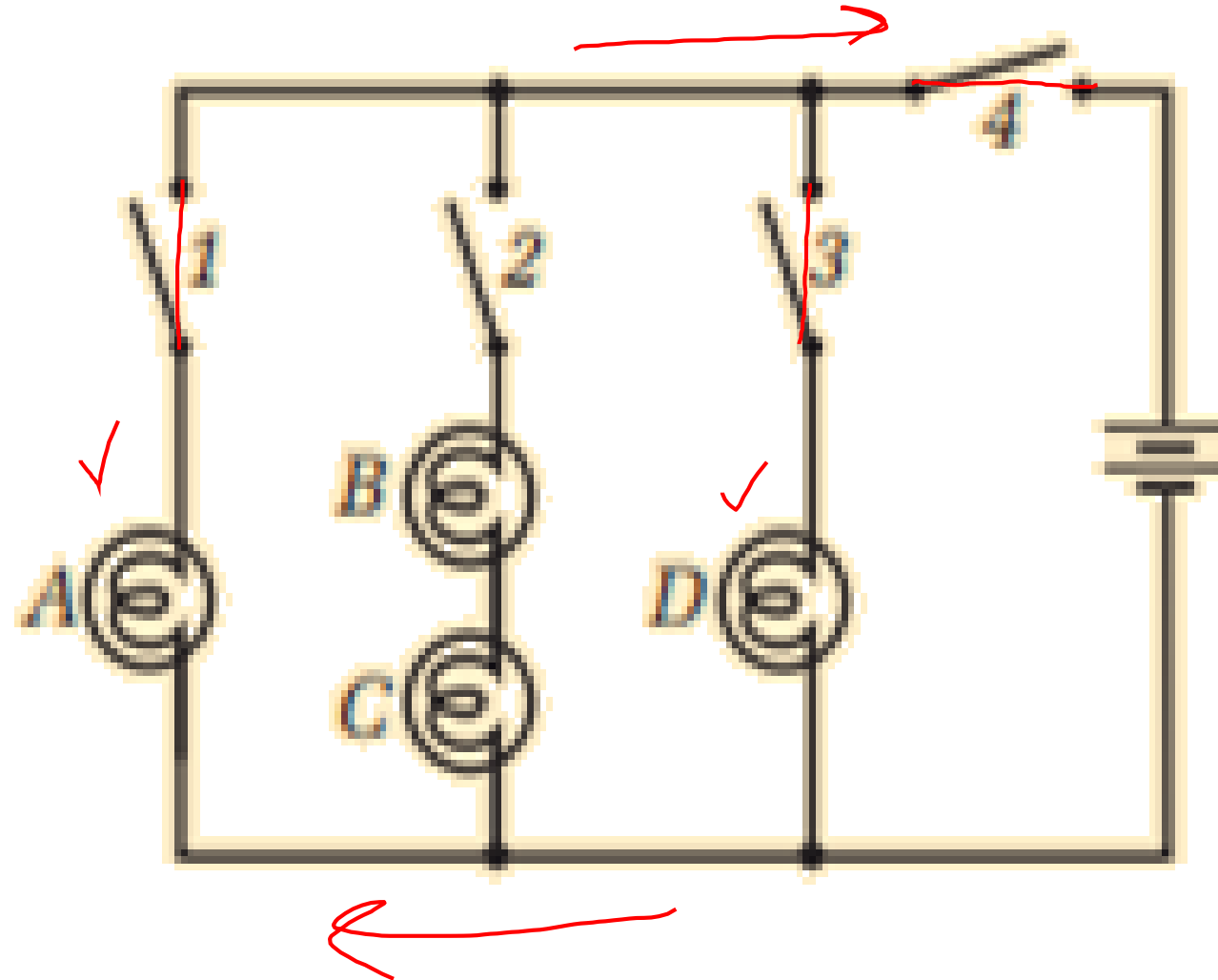
a.) Which switch(es) should be closed to light bulbs A and D only? 1,3,4



The circuit below has four bulbs (A-D) and four switches (1-4).


b.) Which switch(es) should be closed to light bulb A only?

1, 4

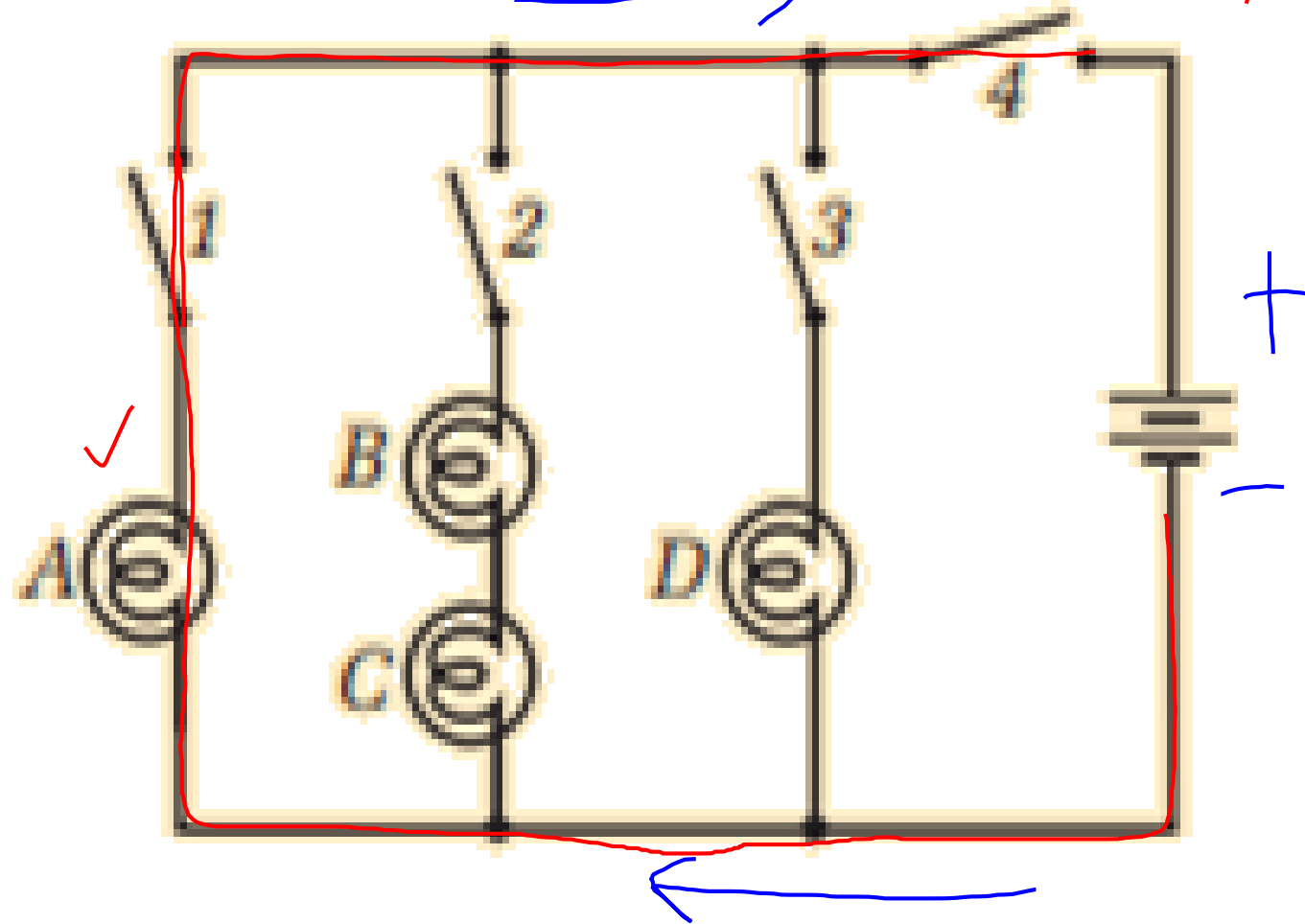


The circuit below has four bulbs (A-D) and four switches (1-4).

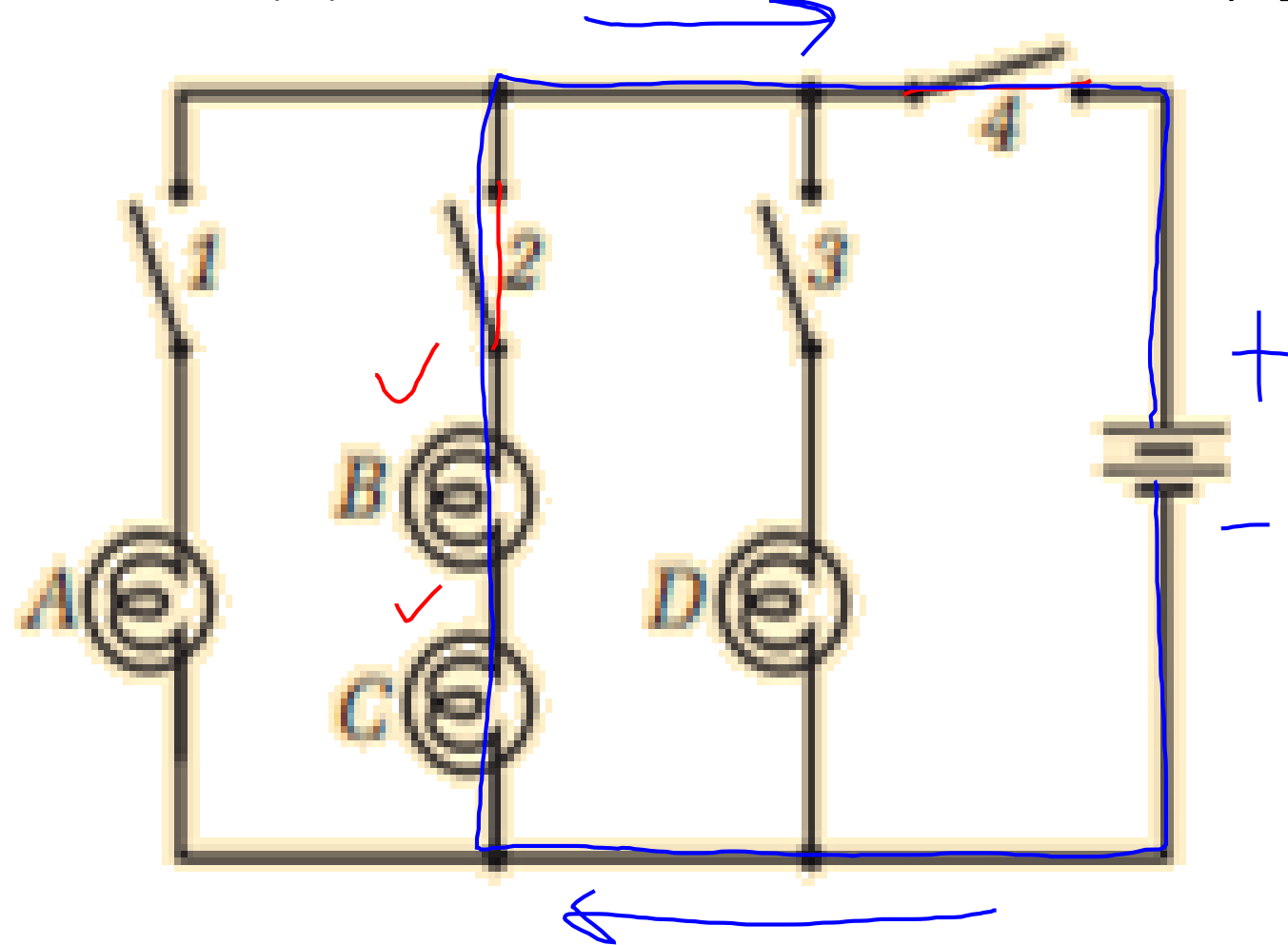c.) Which switch(es) should be closed to light bulbs B and C only? 2, 4



The circuit below has four bulbs (A-D) and four switches (1-4).

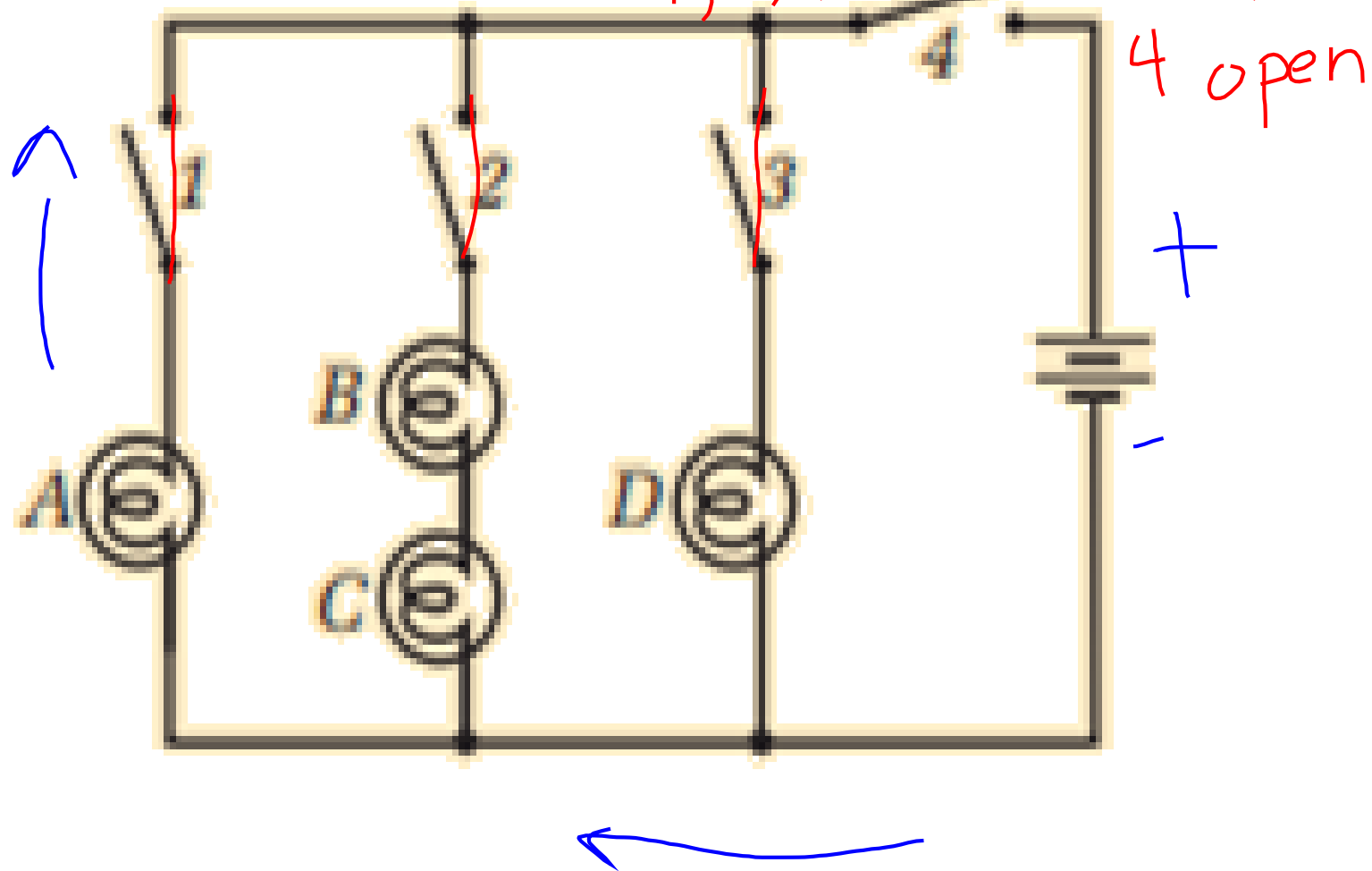
d.) How would you organize the switches so that you could turn all the lights on and off with a single switch? *1, 2, 3 closed and leave 4 open*



The circuit below has four bulbs (A-D) and four switches (1-4).

e.) Is it possible to operate bulbs B and C independently of each other?
Explain

No,
because
B and C
are in

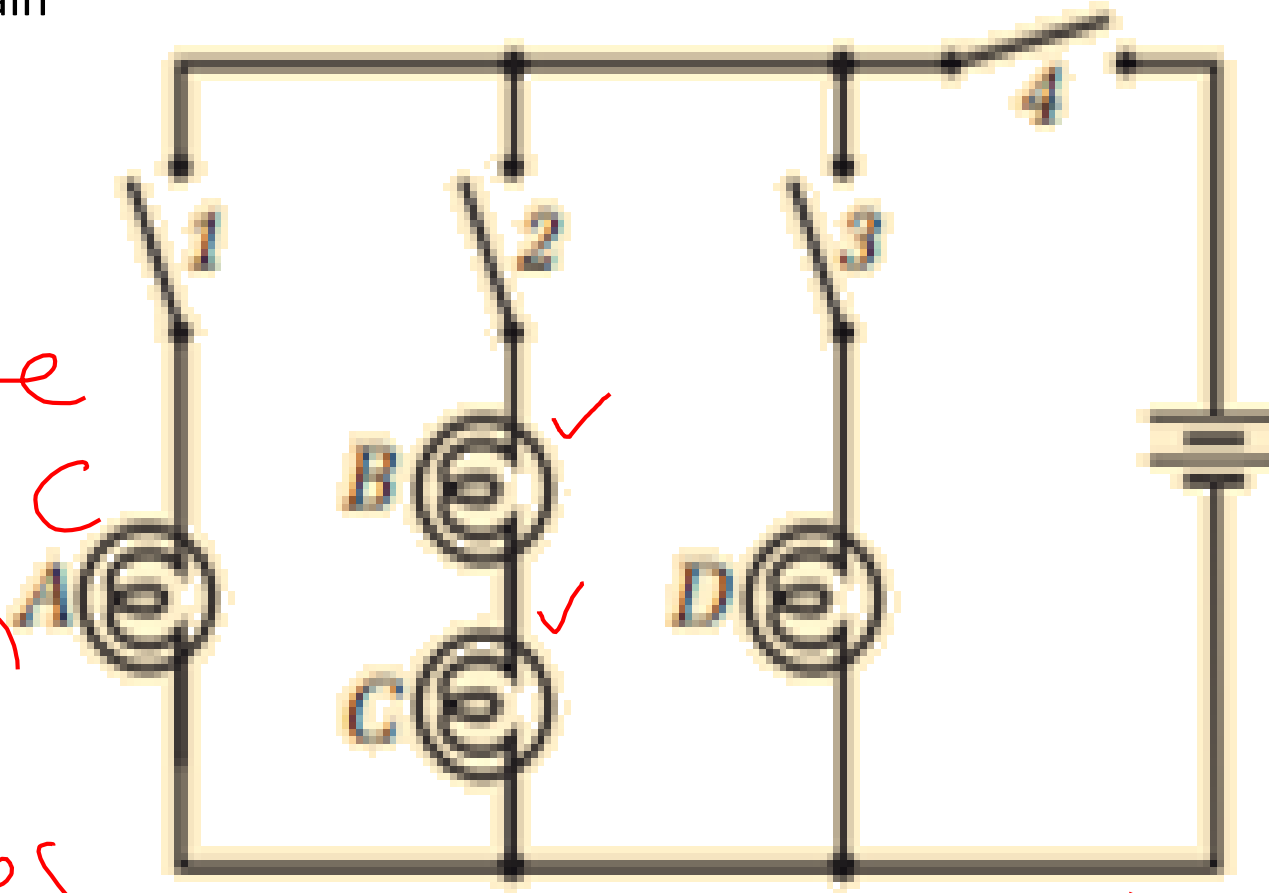

series.

What happens to one also happens to the other.

4. A circuit was made with 3 cells, each with a voltage of 2.0 V. There were 2 lamps connected in parallel. An ammeter was connected right after the battery and read 5.8 A. There was also a resistor connected in series with both lamps.

- Draw the circuit and indicate the direction of electron flow
- Calculate the resistance of the circuit at the point of the ammeter

